 


下る。



Notes:

- RST2_L is system reset synchronized to CLK2. RST1_L is system reset synchronized to CLK1. CLK_SEL is an asynchronous signal.

Figure 2a

Synthesized (gate implementation) schematic from Verilog RTL


 


Figure 2b

 

Notes:

- RST2_L is system reset synchronized to CLK2. RST1_L is system reset synchronized to CLK1. CLK_SEL is an asynchronous signal.

Figure 2c

 


Figure 3

 


Figure 4

 


Figure 5